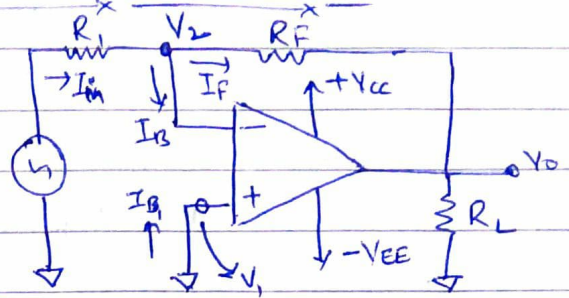



Inverting Input Terminal at virtual Ground



In figure the non-inverting terminal is grounded and the signal is applied to the inverting terminal via resistor R . However, as the difference input voltage is ideally zero: that is, the voltage at the inverting terminal (V_2) is approximately equal to that at the noninverting terminal (V_1). In other words, the inverting terminal voltage V_2 is approximately at ground potential. Therefore the inverting terminal is said to be virtual ground.

$$V_1 = V_2 = 0V$$

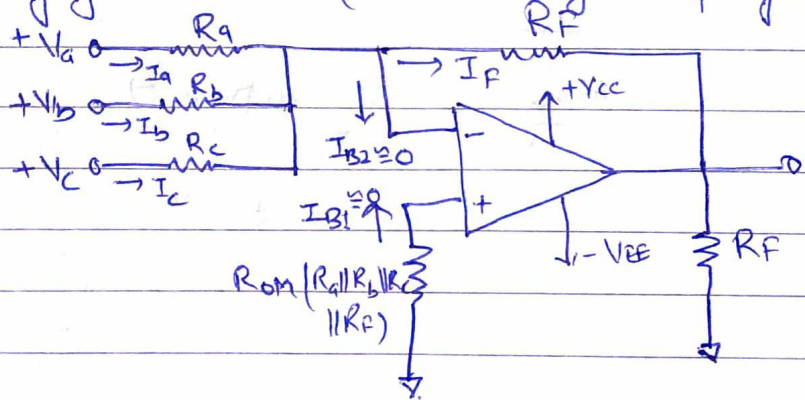Inverting Configuration (Summing Amplifier)



$$I_a + I_b + I_c = I_B + I_F$$

Since R_i and A of the op-amp are ideally infinity

$$I_B = 0A \text{ and } V_1 = V_2 = 0V$$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = -\frac{V_o}{R_f}$$

$$V_o = - \left(\frac{R_F}{R_a} V_a + \frac{R_F}{R_b} V_b + \frac{R_F}{R_c} V_c \right) \quad \text{--- (1)}$$

(a) Summing amplifier
When $R_a = R_b = R_c = R$.

$$V_o = - \frac{R_F}{R} (V_a + V_b + V_c) \quad \text{--- (2)}$$

Where $-\frac{R_F}{R}$ is gain of the circuit.

$$R_a = R_b = R_c = R_F$$

$$\boxed{V_o = - (V_a + V_b + V_c)}$$

(b) Average circuit


$$\text{When } \frac{R_F}{R} = \frac{1}{n}$$

eg (2)

$$n = 3$$

$$V_o = - \frac{(V_a + V_b + V_c)}{3}$$

Non inverting Configuration →

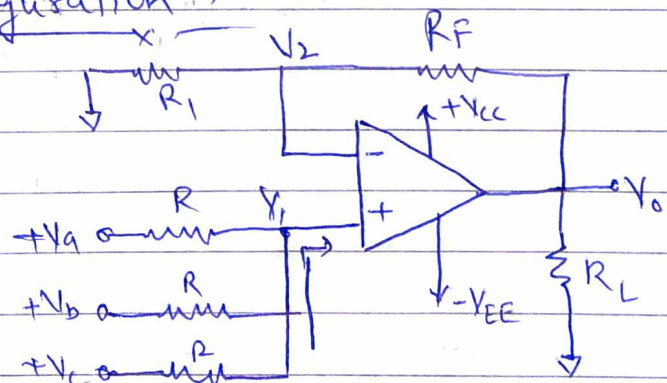

At non-inverting terminal

$$V_i = \frac{R/2}{R+R/2} V_a + \frac{R/2}{R+R/2} V_b + \frac{R/2}{R+R/2} V_c$$

($R/2$ is \parallel combination resistance)

$$V_i = \frac{R/2}{3} \frac{V_a + V_b + V_c}{3} = \frac{1}{3} (V_a + V_b + V_c)$$

The output voltage V_o is

$$\begin{aligned} V_o &= \left(1 + \frac{R_F}{R_i}\right) V_i \\ &= \left(1 + \frac{R_F}{R_i}\right) \left(\frac{V_a + V_b + V_c}{3}\right) \quad \text{--- (1)} \end{aligned}$$

(a) Averaging amplifier

if gain is 1, the output voltage will be equal to the average of all input voltage.

(b) Summing amplifier.


$$\Rightarrow \left(1 + \frac{R_F}{R_i}\right) = 3$$

that is from eq (1)

$$V_o = V_a + V_b + V_c$$

Differential Configuration.

(a) Subtractor.

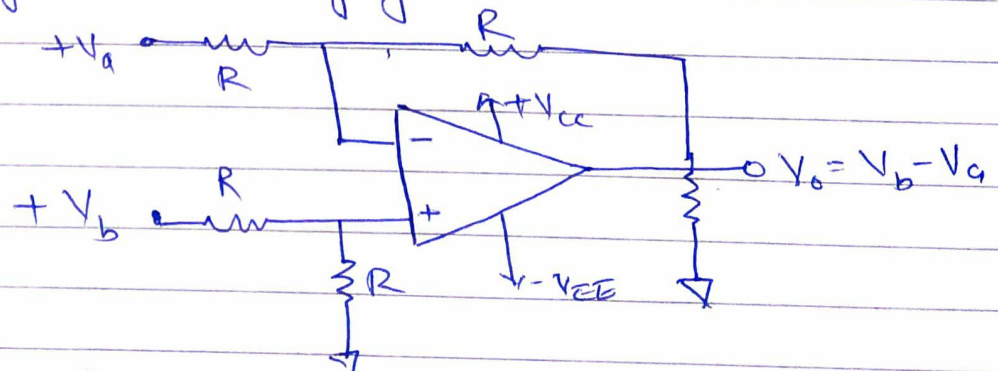


The output voltage of the diff. amp. with a gain 1 is.

$$V_o = -\frac{R}{R} (V_a - V_b)$$

That is $V_o = V_b - V_a$

② Summing amplifier.

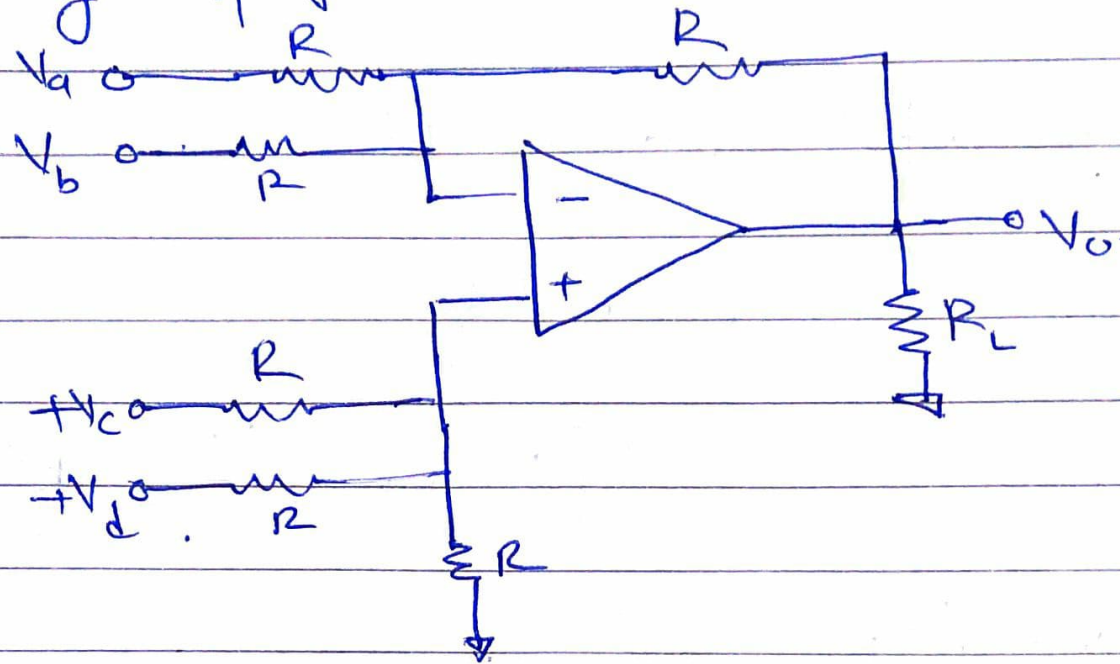

$$V_o = -V_a - V_b + V_c + V_d$$

The output voltage eq for this circuit can be obtained by using the superposition theorem.